

Alexander Hay
ME333 - Mechatronics
Chapter 24.1.2, 24.2.1 and 2,
24.3.1 and 2,

24.1.2 I chose R to be 333Ω by placing three (3) $10k\Omega$ resistors in parallel. Using the materials provided a resistance of 303Ω by placing all resistors in parallel, but that's hard to work with on a breadboard given the difference 30Ω made.

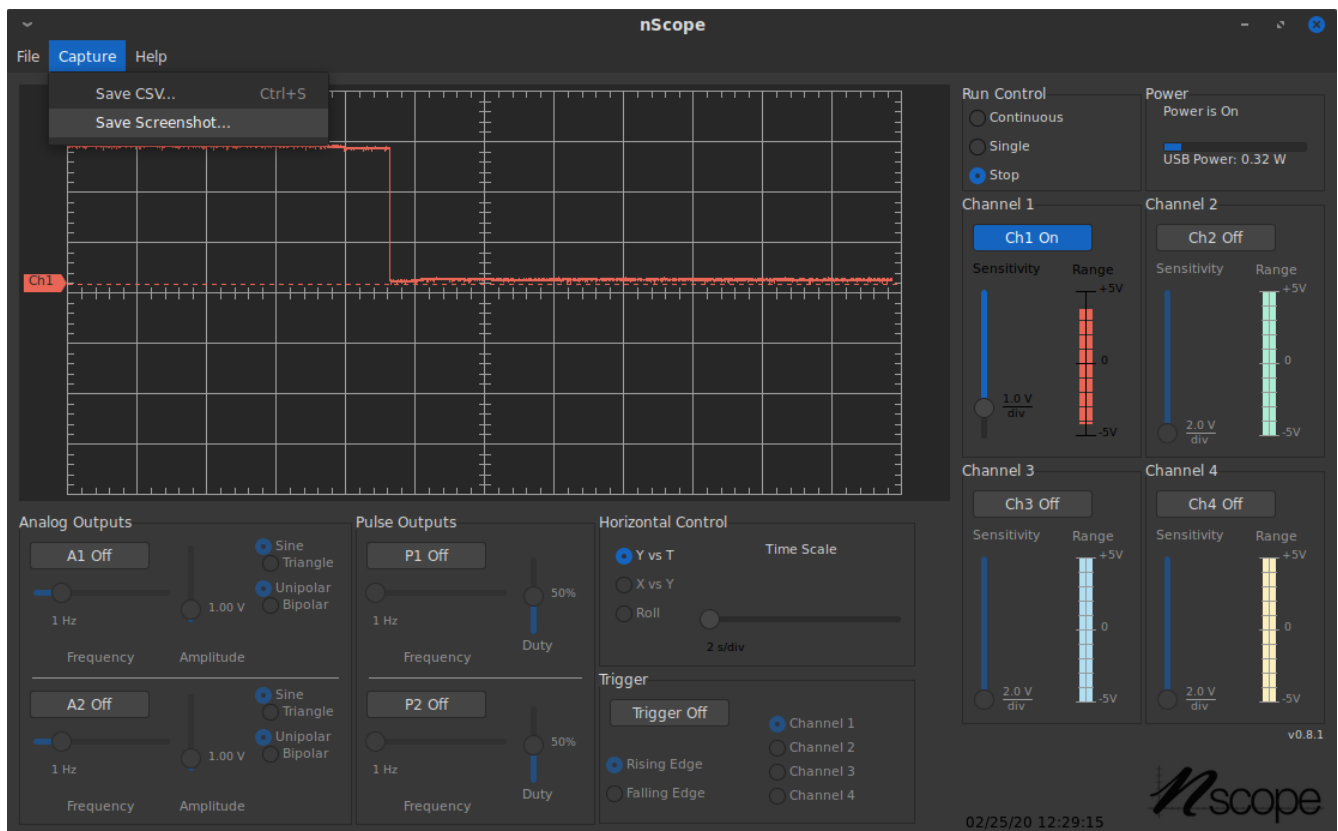


Figure 1: Voltage resting at 3V when LED is on, 0V when the LED is off

24.2.1 $(PR+1)*N*12.5 = \text{period}$

$N = 1$

period = 50

$PR = 3,999$

24.2.2 a

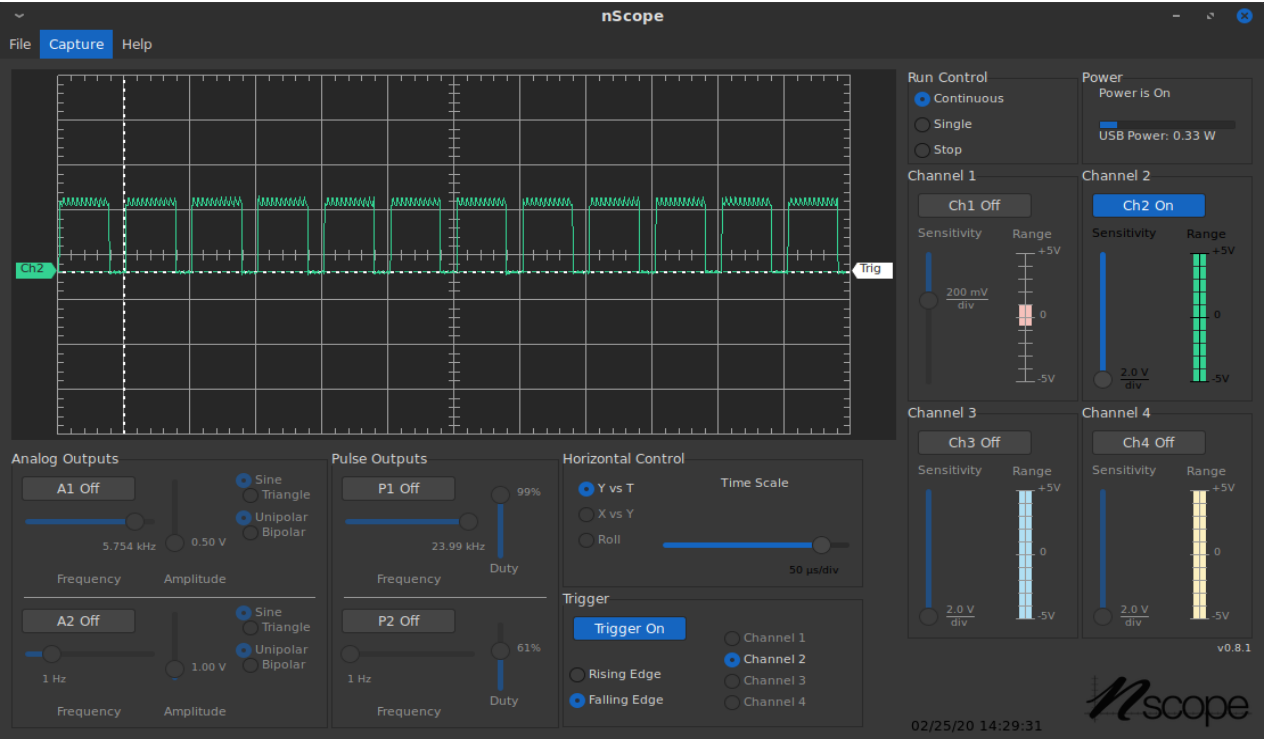


Figure 2: nScope showing square 20kHz wave form at 75% duty cycle

b

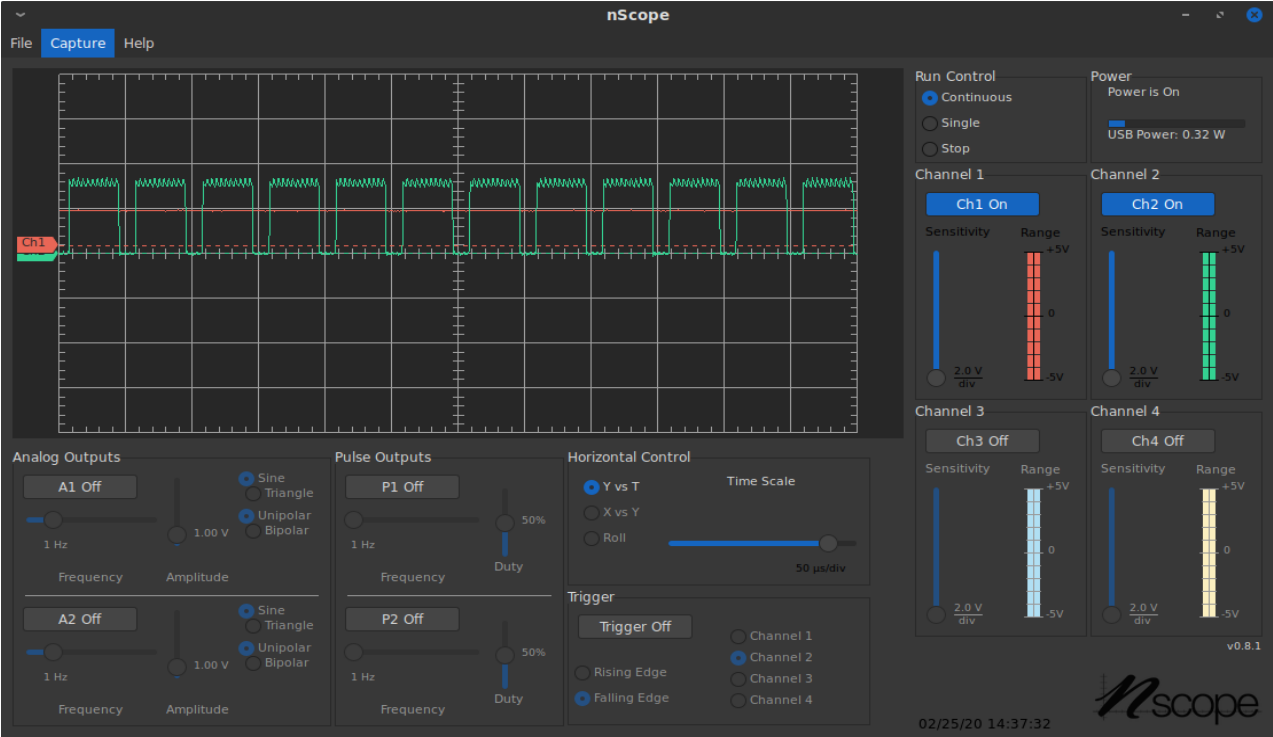


Figure 3: nScope showing waveform and Vout voltage

24.2.2 c Capacitors resist change in voltage so during the low part of the duty cycle the capacitor discharges and has a stabilizing effect on V_{out} .

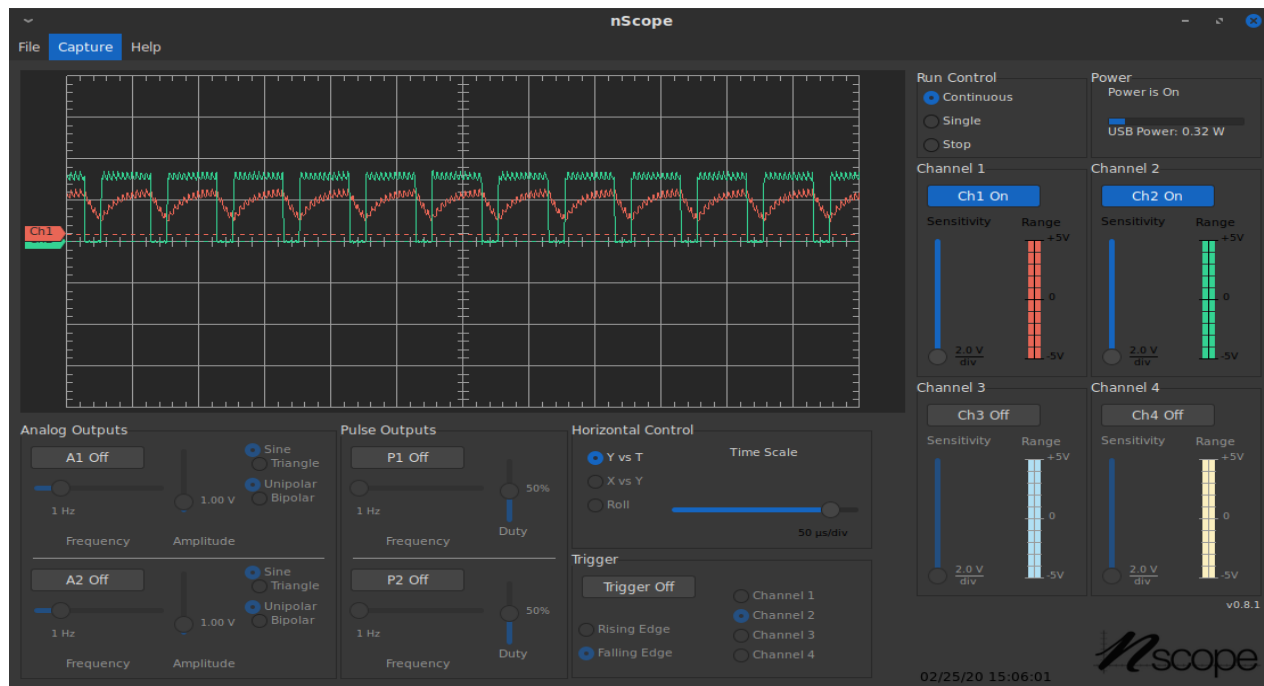


Figure 4: nScope view with capacitor removed

24.3.1

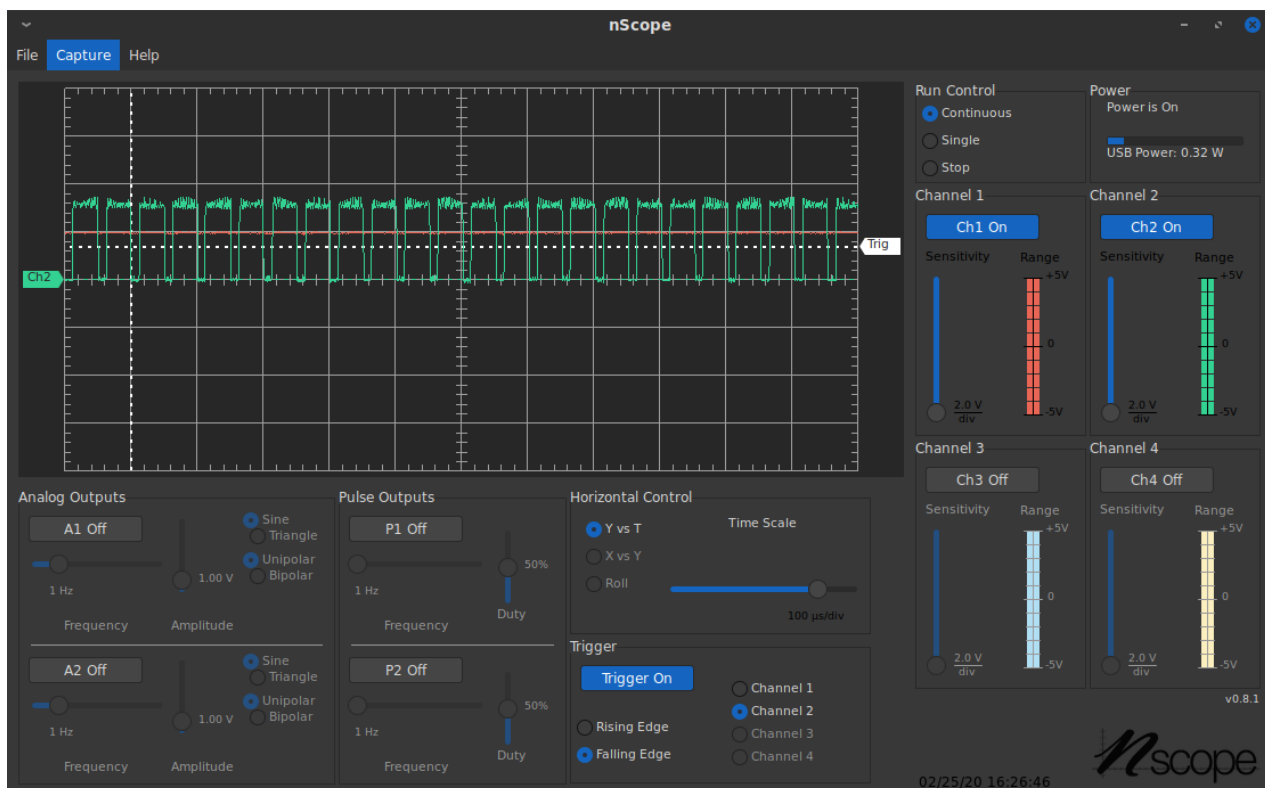


Figure 5: nScope view showing square waveform using interrupts